

---

# REMOTE DISPLAY

## **-LED Matrix-**

---

By : Ashwini Kumar Gupta

B. Engg Electronics & Telecommunication

August 12, 2019



# Contents

<b>1</b>	<b>Project Description</b>	<b>1</b>
1.1	Introduction . . . . .	1
1.2	Feature and Functionality . . . . .	1
1.3	Hardware . . . . .	1
1.3.1	MCU . . . . .	1
1.3.2	LED Matrix . . . . .	2
1.3.3	Power supply . . . . .	2
1.3.4	Input . . . . .	2
<b>2</b>	<b>List Of Tools</b>	<b>3</b>
2.1	Introduction . . . . .	3
<b>3</b>	<b>Hardware</b>	<b>4</b>
3.1	Introduction . . . . .	4
3.2	Control Unit . . . . .	4
3.2.1	MCU . . . . .	4
3.2.2	Oscillator Circuit . . . . .	5
3.2.3	Reset . . . . .	7
3.2.4	Port Assignment . . . . .	8
3.2.5	Voltage Level Indicator . . . . .	8
3.2.6	Display Intensity controller . . . . .	8
3.3	Power Supply . . . . .	8
3.3.1	Power Switch . . . . .	8
3.3.2	Capacitive Power Supply . . . . .	8
3.3.3	Filter . . . . .	8
3.3.4	voltage Regulation . . . . .	8
3.3.5	Current Consumption . . . . .	8
3.4	LED Matrix . . . . .	8
3.4.1	LED . . . . .	8
3.4.2	Transistors . . . . .	8
3.4.3	Shift Registers . . . . .	8
3.5	Input . . . . .	8

<b>4</b>	<b>Software</b>	<b>9</b>
4.1	Introduction . . . . .	9
<b>5</b>	<b>PCB Design</b>	<b>10</b>
5.1	Introduction . . . . .	10
5.2	Crystal . . . . .	10
5.3	Reset . . . . .	10
<b>6</b>	<b>Mechanical CAD</b>	<b>11</b>
6.1	Introduction . . . . .	11
<b>A</b>	<b>Crystal</b>	<b>12</b>
<b>B</b>	<b>Title of app</b>	<b>22</b>
	<b>Acronyms</b>	<b>14</b>

# List of Figures

1	Block Diagram V1.0 . . . . .	2
2	Required Hardware Interface to Micro-controller Unit (MCU) . . . . .	4
3	Oscillator Circuit . . . . .	7
4	Reset Circuit . . . . .	8

# List of Tables

1	Feature and Functionality . . . . .	1
2	Required Hardware Interface to MCU . . . . .	6
3	Crystal Properties(cite datasheet) . . . . .	7

# 1 Project Description

## 1.1 Introduction

THE Remote Display utilises a simple static scrolling Light Emitting Diode (LED) display and makes it accessible from a nearby location using the Bluetooth Low Energy (BLE) feature of an Android phone. Using such a feature the user can modify the display at will and with ease, this reduces the time to manually reprogram the controlling unit and does not require any computer. Having remote access makes the display very handy for a users who keeps the display at a non accessible location.

## 1.2 Feature and Functionality

The Remote Display has following features and functionality.

Table 1: Feature and Functionality

Feature	Functionality
<b>BLE</b>	Provide remote Access
<b>USB</b>	Communicate with computer
<b>BLE LED</b>	BLE status indicator
<b>Speed Controller</b>	Control scrolling speed
<b>Parameter Mode</b>	To edit control parameters

## 1.3 Hardware

### 1.3.1 MCU

The remote display is built around a ATmega328P Alf and Vegard's RISC (AVR) microcontroller. This MCU is based on advanced Reduced Instruction Set Computer (RISC) [?] architecture, 8 bit MCU and 23 programmable Input and Output Line (I/O) lines. For controlling the REMOTE DISPLAY shift registers

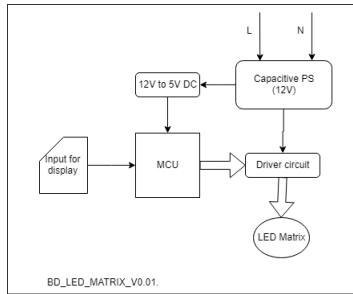


Figure 1: Block Diagram V1.0

are used, 2 for Column and 1 for row, due to shift registers few MCU I/O lines are used.

### 1.3.2 LED Matrix

Single colour red 5mm LED used to build the matrix, total of 128 LED required for 16x8 matrix. An array of transistors configured as switch to provide required current for each row of LED matrix.

### 1.3.3 Power supply

The project utilises a transformerless capacitive power supply design. Such a design is helpful in

reducing the overall cost of project and also utilises fewer components thus saving space and cost.

### 1.3.4 Input

The project is aimed to dynamically modify the display commands through an input source like computer or BLE, through Universal Synchronous Asynchronous Receiver Transmitter (USART). Such a feature helps in modifying the display at will rather than modifying the source code.





## **2 List Of Tools**

### **2.1 Introduction**

Enter some text here



## 3 Hardware

### 3.1 Introduction

Enter some text here

### 3.2 Control Unit


#### 3.2.1 MCU

#### Selecting the MCU

Step 1: *Make a list of required hardware interfaces*      Step 2: *Examine the architecture*

To select a particular MCU, the required hardware interfacing is mandatory because hardware interface defines the required peripherals and General Purpose Input and Output (GPIO). The list of hardware interface in this project is provided in Table 2(also refer 2).

Figure 2: Required Hardware Interface to MCU

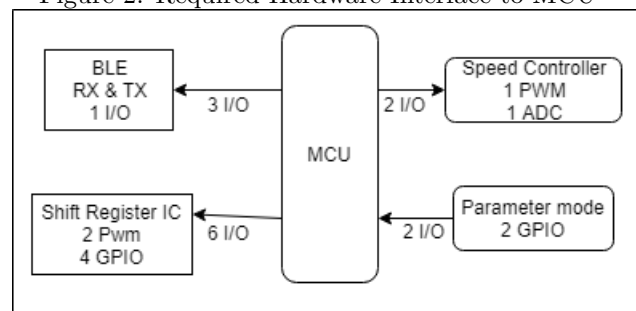

The project requires fast execution of instruction and repetitive access to memory due to use of communication protocols and USART peripheral. The **Harvard architecture** suites this application more than the Von-Neuman architecture, since Harvard architecture has dedicated buses for different sections of MCU

and has pipeline instruction set feature, thus executing more instructions than Von-Neuman architecture in a given period of time. The MCU should have be either 8 bit or 16 bit, since the application does not require high and complex processing. A 8 bit MCU supporting few Mhz of frequency will also suit this application.

#### Step 3: *Identify Memory Needs*

This project would require the following minimum memory(as per rough calculations).

EEPROM : 1 KB

Flash : 16 KB

SRAM : 512 Bytes

#### Step 4: *Searching for MCU*

Selecting MCU as per above parameters, AVR series from Atmel crop and MSP40 series of Texas Instruments are good options.considering future enhancement, cost, development kits, support for MCU and development platform (like IDE and drivers) the AVR series ATmega328P is selected.

#### **ATmega328P**

The MCU is the central processing unit of the system. For this application/project the ATmega328P, by Atmel Corporation is selcted. Following is the list of features [?].

- Advanced RISC architecture
- 32K bytes of in-system self-programmable flash program memory.
- 1Kbytes Electrically Erasable Programmable Read-Only Memory (EEPROM).

- 2Kbytes Static Random Access Memory (SRAM).
- Two 8-bit Timer/Counters
- One 16-bit Timer/Counter
- Six Pulse Width Modulation (PWM) channels
- 8-channel 10-bit Analog to Digital Converter (ADC)
- USART
- Master/slave Serial Peripheral Interface (SPI)
- Inter-Integrated Circuit (I2C)
- watchdog timer
- On-chip analog comparator
- Six sleep modes

#### **3.2.2 Oscillator Circuit**

**The** oscillator circuit is required for generating clock for MCU.Accuracy of timing application is dependent on the accuracy of the oscillator provided in the MCU. The oscillators supported by ATmega328P are listed below [?].

- Low power crystal oscillator
- **Full swing crystal oscillator**
- Low frequency crystal oscillator
- Internal 128 Kilo Hertz (KHz) RC oscillator
- Calibrated internal RC oscillator
- External clock

**For** this application the MCU will be in Full swing crystal oscillator mode.

Table 2: Required Hardware Interface to MCU

Sr. no.	Interface	GPIO	PWM	ADC	USART	Remark
1	BLE	0	0	0	1	RX and TX
2	BLE LED	1	0	0	0	Show BLE status
3	Speed Control	0	1	1	0	Control scrolling speed
4	Parameter mode	2	0	0	0	Edit parameters
5	Serial Interface	0	0	0	1	RX and TX Multiplexed with BLE
6	IC 74HC595	4	2	0	0	1 Row 2 Col
	<b>Total</b>	<b>7</b>	<b>3</b>	<b>1</b>	<b>1</b>	<b>12</b>

**Advantages:**

- 16 Mega Hertz (MHz).
- rail to rail swing.
- Drive other clock sources
- Less effect of noisy environment

**Disadvantages:**

- Higher current consumption than Low power crystal oscillator.(Power consumed by a crystal is not very significant, since using a 230 V AC source.)
- Operating Voltage of MCU becomes 2.7 V to 5.00 V.(MCU will be working on 5 V DC which is within the operating voltage defined.)

- Mode of operation : Fundamental
- Resonant: Parallel
- Tolerance: 0 - 50 ppm
- Temperature Stability: 0 - 50 ppm
- Equivalent Series Resistance (ESR): 60 to 100  $\Omega$
- Package type : Surface Mount Technology (SMT) , since such crystals provide with less stray capacitance.

**Selected Crystal** is TSX-3225 16.0000MF09Z-AC0 a SMT 4 pin device package. Refer 3 for details.

**Selecting Crystal****Oscillator Circuit Design****Crystal Requirement****1. Load Capacitors:**

- Frequency: 16 MHz
- $C_L$ : 6 - 11 pF [?]
- $C_1$  and  $C_2$  together act as load capacitance.

Figure 3: Oscillator Circuit

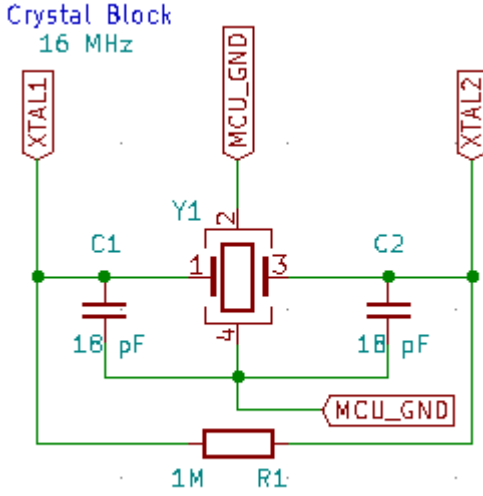


Table 3: Crystal Properties(cite datasheet)

Device Manufacturer	EPSON
Part No.	TSX-3225 16.0000 MF09Z-AC0
Case (mm X mm)	3.2 x 2.5
THT / SMT	SMD
Fundamental Frequency ( MHz)	16
Frequency Stability (ppm)	9
Frequency Tolerance(ppm)	10
$C_L$ pF	9
Operating Temp max(°C )	75
Operating Temp min(°C)	-20
Aging (ppm)	1
ESR (Ω)	60

- To have total 180°shift due to active state.The reset circuit for this MCU is provided in figure 4.(cite avr042 here)

capacitor provides with 90°shift in phase. The value of the load capacitor is provided (cite datasheet).

- $C_L$  (Total Load capacitance) = 9 pF (cite DS)
- $C_s$  : Stray capacitance.
- $C_1, C_2$  are load capacitors
- Considering  $C_1 = C_2$ .
- value of  $C_1$  and  $C_2$  can be calculated using the following equation.

$$C_L = \frac{C_1 C_2}{C_1 + C_2} + C_s \quad (1)$$

$$C_1 = 2(C_L - C_s) \quad (2)$$

- Considering  $C_s = 0$  pF.

$$C_1 = 2(9 - 0) \quad (3)$$

$$C_1 = 18 \text{ pF} \quad (4)$$

- Since crystal has drive level in range of 200  $\mu$  W, 0603 package ,i.e 0.1 W, is selected with value of 18 pF, 0603.
- The resistor  $R_1$  is used to make the behaviour linear, this enhances the output of the crystal circuit.  $R_1 = 1 \text{ M } \Omega$ , 0603.


### Printed Circuit Board (PCB) design.

[?]

#### 3.2.3 Reset

**Reset** logic is used to set the MCU in known state.The reset circuit for this MCU is provided in figure 4.(cite avr042 here)

Figure 4: Reset Circuit

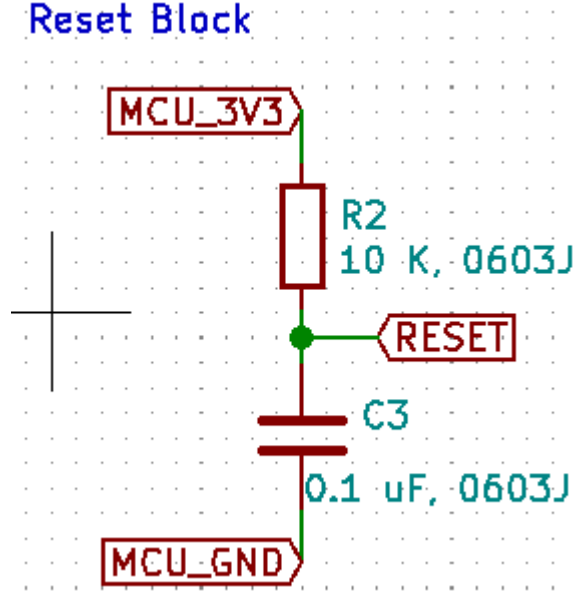

### Value Calculation

**R2** is acting as pull-up resistor here, which is used for high voltage programming (10V - 12V). Recommended value of pull-up resistor is 10 KΩ.

**C3** is used to filter high frequency noise, typical value is 100 nF (or 0.1 μF).

### Power Calculation

Maximum allowable voltage for  $V_{cc}$  is 5.5 V and  $V_{thresh}$  for reset pin detection is 1.1 V (cite datasheet here).

R2: consumes less than 0.1 w(equation 5), using 0603 Surface Mount Devices (SMD) package.

$$P = \frac{V^2}{R}$$

$$V = 5.5V(max)$$

$$R_2 = 10K\Omega$$

$$P = 3.025mW \quad (5)$$

C3: Max current flow through C3 is given by equation 6. Here  $I = 0.55$  mA, Power = 3.025 mW, so using a 0603 SMD package, since 0603

provides with 0.1 W power rating.

$$I = \frac{V}{R_2} \quad (6)$$

$$P = VI$$

$$P = 3.025mW$$

f: The RC circuit also act as a Low Pass Filter (LPF), the cut-off frequency of RC filter is given by equation 7.

$$f = \frac{1}{2\pi RC} \quad (7)$$

$f = 159.15$  Hz, so all high frequency noise is filtered out by this RC filter thus enhancing the performance of MCU in noisy environment and preventing unwanted reset.

### 3.2.4 Port Assignment

### 3.2.5 Voltage Level Indicator

### 3.2.6 Display Intensity controller

## 3.3 Power Supply

### 3.3.1 Power Switch

### 3.3.2 Capacitive Power Supply

### 3.3.3 Filter

### 3.3.4 voltage Regulation

### 3.3.5 Current Consumption

## 3.4 LED Matrix

### 3.4.1 LED

### 3.4.2 Transistors

### 3.4.3 Shift Registers

## 3.5 Input





## 4 Software

### 4.1 Introduction

Enter some text here



# 5 PCB Design

## 5.1 Introduction

Enter some text here

## 5.2 Crystal

Following are the precautions taken while designing layout for crystal oscillator circuit.

1. Crystal placed at very short distance from MCU to avoid stray capacitance.
2. Shielding crystal with ground plane
3. Crystal tracks to be apart from each other,

minimize stray capacitance.

4. Keep clock and high frequency lines far away from crystal.
5. Load  $XTAL_{in}$  capacitor should be closer to  $XTAL_{in}$  pin and ground plane.(cite application note.)

## 5.3 Reset

The reset circuit should be close to RESET pin of MCU, to avoid unwanted noise and stray capacitance.



## 6 Mechanical

## CAD

### 6.1 Introduction

Enter some text here



# A Crystal

some text here

**Selecting** crystal requires following considerations.

1. Through-Hole Technology (THT) or SMT.
2. Load capacitance.
3. Frequency of operation
4. Q - factor
5. ESR
6. Frequency Pulling
7. Drive level
8. Minimum negative Resistance
9. Frequency stability
10. Frequency Tolerance





# **B Title of app 22**

some thext theri



# Acronyms

**ADC** Analog to Digital Converter. 5, 6

**AVR** Alf and Vegard's RISC. 1, 5

**BLE** Bluetooth Low Energy. 1, 2, 6

**EEPROM** Electrically Erasable Programmable  
Read-Only Memory. 5

**ESR** Equivalent Series Resistance. 6, 12

**GPIO** General Purpose Input and Output. 4, 6

**I/O** Input and Output Line. 1, 2

**I2C** Inter-Integrated Circuit. 5

**IC** Integrated Circuits. 6

**KB** Kilo Bytes. 5

**KHz** Kilo Hertz. 5

**LED** Light Emitting Diode. 1, 2, 6

**LPF** Low Pass Filter. 8

**MCU** Micro-controller Unit. iii, iv, 1, 2, 4, 5, 6, 7,  
8, 10

**MHz** Mega Hertz. 6, 7

**PCB** Printed Circuit Board. 7

**ppm** Parts Per Million. 6, 7

**PWM** Pulse Width Modulation. 5, 6

**RISC** Reduced Instruction Set Computer. 1, 5

**RX** Receive Pin. 6

**SMD** Surface Mount Devices. 8

**SMT** Surface Mount Technology. 6, 7, 12

**SPI** Serial Peripheral Interface. 5

**SRAM** Static Random Access Memory. 5

**THT** Through-Hole Technology. 7, 12

**TX** Transmit Pin. 6

**USART** Universal Synchronous Asynchronous  
Receiver Transmitter. 2, 4, 5, 6

**USB** Universal Serial Bus. 1

