
REMOTE DISPLAY

-LED Matrix-

By : Ashwini Kumar Gupta
B. Engg Electronics & Telecommunication
August 11, 2019

Contents

1	Project Description	1
1.1	Introduction	1
1.2	Feature and Functionality	1
1.3	Hardware	1
1.3.1	MCU	1
1.3.2	LED Matrix	2
1.3.3	Power supply	2
1.3.4	Input	2
2	List Of Tools	3
2.1	Introduction	3
3	Hardware	4
3.1	Introduction	4
3.2	Control Unit	4
3.2.1	MCU	4
3.2.2	Oscillator Circuit	5
3.2.3	Reset	7
3.2.4	Port Assignment	8
3.2.5	Voltage Level Indicator	8
3.2.6	Display Intensity controller	8
3.3	Power Supply	8
3.3.1	Power Switch	8
3.3.2	Capacitive Power Supply	8
3.3.3	Filter	8
3.3.4	voltage Regulation	8
3.3.5	Current Consumption	8
3.4	LED Matrix	8
3.4.1	LED	8
3.4.2	Transistors	8
3.4.3	Shift Registers	8
3.5	Input	8

4	Software	9
4.1	Introduction	9
5	PCB Design	10
5.1	Introduction	10
5.2	Crystal	10
6	Mechanical CAD	11
6.1	Introduction	11
A	Crystal	12
B	Title of app	22
	Acronyms	14

List of Figures

1	Block Diagram V1.0	2
2	Required Hardware Interface to Micro-controller Unit (MCU)	4
3	Oscillator Circuit	7
4	Reset Circuit	8

List of Tables

1	Feature and Functionality	1
2	Required Hardware Interface to MCU	6
3	Crystal Properties(cite datasheet)	7

1 Project Description

1.1 Introduction

THE Remote Display utilises a simple static scrolling Light Emitting Diode (LED) display and makes it accessible from a nearby location using the Bluetooth Low Energy (BLE) feature of an Android phone. Using such a feature the user can modify the display at will and with ease, this reduces the time to manually reprogram the controlling unit and does not require any computer. Having remote access makes the display very handy for a users who keeps the display at a non accessible location.

1.2 Feature and Functionality

The Remote Display has following features and functionality.

Table 1: Feature and Functionality

Feature	Functionality
BLE	Provide remote Access
USB	Communicate with computer
BLE LED	BLE status indicator
Speed Controller	Control scrolling speed
Parameter Mode	To edit control parameters

1.3 Hardware

1.3.1 MCU

The remote display is built around a ATmega328P Alf and Vegard's RISC (AVR) microcontroller. This MCU is based on advanced Reduced Instruction Set Computer (RISC) [?] architecture, 8 bit MCU and 23 programmable Input and Output Line (I/O) lines. For controlling the REMOTE DISPLAY shift registers

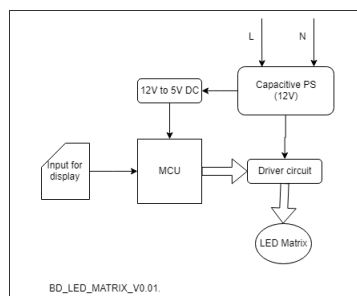


Figure 1: Block Diagram V1.0

are used, 2 for Column and 1 for row, due to shift registers few MCU I/O lines are used.

1.3.2 LED Matrix

Single colour red 5mm LED used to build the matrix, total of 128 LED required for 16x8 matrix. An array of transistors configured as switch to provide required current for each row of LED matrix.

1.3.3 Power supply

The project utilises a transformerless capacitive power supply design. Such a design is helpful in

reducing the overall cost of project and also utilises fewer components thus saving space and cost.

1.3.4 Input

The project is aimed to dynamically modify the display commands through an input source like computer or BLE, through Universal Synchronous Asynchronous Receiver Transmitter (USART). Such a feature helps in modifying the display at will rather than modifying the source code.

2 List Of Tools

2.1 Introduction

Enter some text here

3 Hardware

3.1 Introduction

Enter some text here

3.2 Control Unit


3.2.1 MCU

Selecting the MCU

Step 1: *Make a list of required hardware interfaces* Step 2: *Examine the architecture*

To select a particular MCU, the required hardware interfacing is mandatory because hardware interface defines the required peripherals and General Purpose Input and Output (GPIO). The list of hardware interface in this project is provided in Table 2(also refer 2).

Figure 2: Required Hardware Interface to MCU

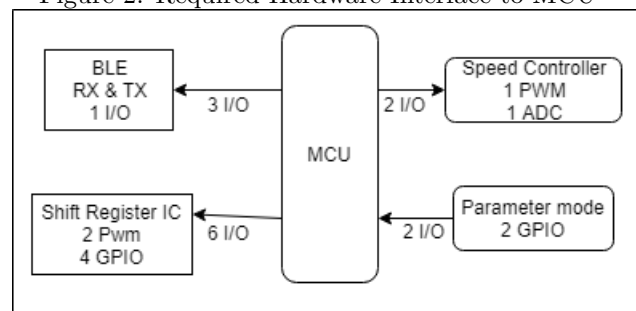

The project requires fast execution of instruction and repetitive access to memory due to use of communication protocols and USART peripheral. The **Harvard architecture** suites this application more than the Von-Neuman architecture, since Harvard architecture has dedicated buses for different sections of MCU

and has pipeline instruction set feature, thus executing more instructions than Von-Neuman architecture in a given period of time. The MCU should have be either 8 bit or 16 bit, since the application does not require high and complex processing. A 8 bit MCU supporting few Mhz of frequency will also suit this application.

Step 3: *Identify Memory Needs*

This project would require the following minimum memory(as per rough calculations).

EEPROM : 1 KB

Flash : 16 KB

SRAM : 512 Bytes

Step 4: *Searching for MCU*

Selecting MCU as per above parameters, AVR series from Atmel crop and MSP40 series of Texas Instruments are good options.considering future enhancement, cost, development kits, support for MCU and development platform (like IDE and drivers) the AVR series ATmega328P is selected.

ATmega328P

The MCU is the central processing unit of the system. For this application/project the ATmega328P, by Atmel Corporation is selcted. Following is the list of features [?].

- Advanced RISC architecture
- 32K bytes of in-system self-programmable flash program memory.
- 1Kbytes Electrically Erasable Programmable Read-Only Memory (EEPROM).

- 2Kbytes Static Random Access Memory (SRAM).
- Two 8-bit Timer/Counters
- One 16-bit Timer/Counter
- Six Pulse Width Modulation (PWM) channels
- 8-channel 10-bit Analog to Digital Converter (ADC)
- USART
- Master/slave Serial Peripheral Interface (SPI)
- Inter-Integrated Circuit (I2C)
- watchdog timer
- On-chip analog comparator
- Six sleep modes

3.2.2 Oscillator Circuit

The oscillator circuit is required for generating clock for MCU.Accuracy of timing application is dependent on the accuracy of the oscillator provided in the MCU. The oscillators supported by ATmega328P are listed below [?].

- Low power crystal oscillator
- **Full swing crystal oscillator**
- Low frequency crystal oscillator
- Internal 128 Kilo Hertz (KHz) RC oscillator
- Calibrated internal RC oscillator
- External clock

For this application the MCU will be in Full swing crystal oscillator mode.

Table 2: Required Hardware Interface to MCU

Sr. no.	Interface	GPIO	PWM	ADC	USART	Remark
1	BLE	0	0	0	1	RX and TX
2	BLE LED	1	0	0	0	Show BLE status
3	Speed Control	0	1	1	0	Control scrolling speed
4	Parameter mode	2	0	0	0	Edit parameters
5	Serial Interface	0	0	0	1	RX and TX Multiplexed with BLE
6	IC 74HC595	4	2	0	0	1 Row 2 Col
	Total	7	3	1	1	12

Advantages:

- 16 Mega Hertz (MHz).
- rail to rail swing.
- Drive other clock sources
- Less effect of noisy environment

Disadvantages:

- Higher current consumption than Low power crystal oscillator.(Power consumed by a crystal is not very significant, since using a 230 V AC source.)
- Operating Voltage of MCU becomes 2.7 V to 5.00 V.(MCU will be working on 5 V DC which is within the operating voltage defined.)

- Mode of operation : Fundamental
- Resonant: Parallel
- Tolerance: 0 - 50 ppm
- Temperature Stability: 0 - 50 ppm
- Equivalent Series Resistance (ESR): 60 to 100 Ω
- Package type : Surface Mount Technology (SMT) , since such crystals provide with less stray capacitance.

Selected Crystal is TSX-3225 16.0000MF09Z-AC0 a SMT 4 pin device package. Refer 3 for details.

Selecting Crystal**Oscillator Circuit Design****Crystal Requirement****1. Load Capacitors:**

- Frequency: 16 MHz
- C_L : 6 - 11 pF [?]
- C_1 and C_2 together act as load capacitance.

Figure 3: Oscillator Circuit

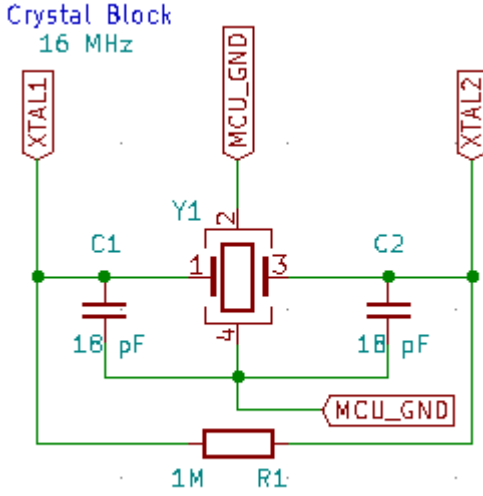


Table 3: Crystal Properties(cite datasheet)

Device Manufacturer	EPSON
Part No.	TSX-3225 16.0000 MF09Z-AC0
Case (mm X mm)	3.2 x 2.5
THT / SMT	SMD
Fundamental Frequency (MHz)	16
Frequency Stability (ppm)	9
Frequency Tolerance(ppm)	10
C_L pF	9
Operating Temp max(°C)	75
Operating Temp min(°C)	-20
Aging (ppm)	1
ESR (Ω)	60

- To have total 180°shift due to active state.The reset circuit for this MCU is provided in figure 4.(cite avr042 here)

capacitor provides with 90°shift in phase. The value of the load capacitor is provided (cite datasheet).

- C_L (Total Load capacitance) = 9 pF (cite DS)
- C_s : Stray capacitance.
- C_1, C_2 are load capacitors
- Considering $C_1 = C_2$.
- value of C_1 and C_2 can be calculated using the following equation.

$$C_L = \frac{C_1 C_2}{C_1 + C_2} + C_s \quad (1)$$

$$C_1 = 2(C_L - C_s) \quad (2)$$

- Considering $C_s = 0$ pF.

$$C_1 = 2(9 - 0) \quad (3)$$

$$C_1 = 18 \text{ pF} \quad (4)$$

- Since crystal has drive level in range of 200 μ W, 0603 package ,i.e 0.1 W, is selected with value of 18 pF, 0603.
- The resistor R_1 is used to make the behaviour linear, this enhances the output of the crystal circuit. $R_1 = 1 \text{ M } \Omega$, 0603.


Printed Circuit Board (PCB) design.

[?]

3.2.3 Reset

Reset logic is used to set the MCU in known state.The reset circuit for this MCU is provided in figure 4.(cite avr042 here)

Figure 4: Reset Circuit

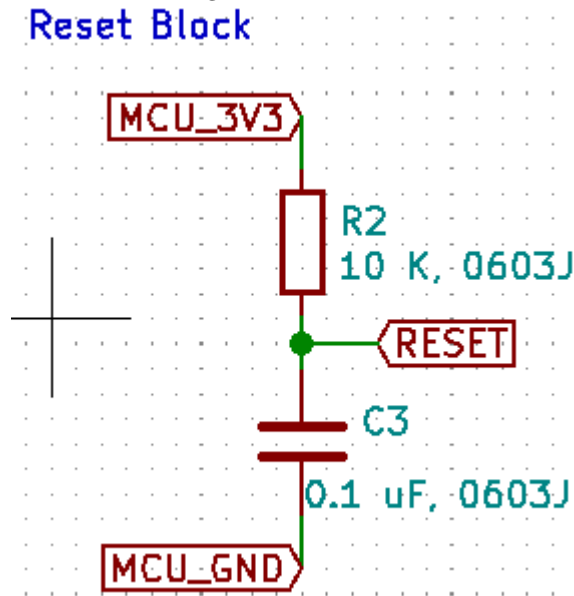

Value Calculation

R2 is acting as pull-up resistor here, which is used for high voltage programming (10V - 12V). Recommended value of pull-up resistor is 10 K Ω .

C3 is used to filter high frequency noise, typical value is 100 nF (or 0.1 μ F).

Power Calculation

Maximum allowable voltage for V_{cc} is 5.5 V and V_{thresh} for reset pin detection is 1.1 V (cite datasheet

here).

R1:

$$n = m$$

3.2.4 Port Assignment

3.2.5 Voltage Level Indicator

3.2.6 Display Intensity controller

3.3 Power Supply

3.3.1 Power Switch

3.3.2 Capacitive Power Supply

3.3.3 Filter

3.3.4 voltage Regulation

3.3.5 Current Consumption

3.4 LED Matrix

3.4.1 LED

3.4.2 Transistors

3.4.3 Shift Registers

3.5 Input

4 Software

4.1 Introduction

Enter some text here

5 PCB

Design

5.1 Introduction

Enter some text here

5.2 Crystal

Following are the precautions taken while designing layout for crystal oscillator circuit.

1. Crystal placed at very short distance from MCU to avoid stray capacitance.

2. Shielding crystal with ground plane
3. Crystal tracks to be apart from each other, minimize stray capacitance.
4. Keep clock and high frequency lines far away from crystal.
5. Load $XTAL_{in}$ capacitor should be closer to $XTAL_{in}$ pin and ground plane.(cite application note.)

6 Mechanical

CAD

6.1 Introduction

Enter some text here

A Crystal

some text here

Selecting crystal requires following considerations.

1. Through-Hole Technology (THT) or SMT.
2. Load capacitance.
3. Frequency of operation
4. Q - factor
5. ESR
6. Frequency Pulling
7. Drive level
8. Minimum negative Resistance
9. Frequency stability
10. Frequency Tolerance

B Title of app 22

some thext theri

Acronyms

ADC Analog to Digital Converter. 5, 6

AVR Alf and Vegard's RISC. 1, 5

BLE Bluetooth Low Energy. 1, 2, 6

EEPROM Electrically Erasable Programmable
Read-Only Memory. 5

ESR Equivalent Series Resistance. 6, 12

GPIO General Purpose Input and Output. 4, 6

I/O Input and Output Line. 1, 2

I2C Inter-Integrated Circuit. 5

IC Integrated Circuits. 6

KB Kilo Bytes. 5

KHz Kilo Hertz. 5

LED Light Emitting Diode. 1, 2, 6

MCU Micro-controller Unit. iii, iv, 1, 2, 4, 5, 6, 7,
10

MHz Mega Hertz. 6, 7

PCB Printed Circuit Board. 7

ppm Parts Per Million. 6, 7

PWM Pulse Width Modulation. 5, 6

RISC Reduced Instruction Set Computer. 1, 5

RX Receive Pin. 6

SMT Surface Mount Technology. 6, 7, 12

SPI Serial Peripheral Interface. 5

SRAM Static Random Access Memory. 5

THT Through-Hole Technology. 7, 12

TX Transmit Pin. 6

USART Universal Synchronous Asynchronous
Receiver Transmitter. 2, 4, 5, 6

USB Universal Serial Bus. 1

